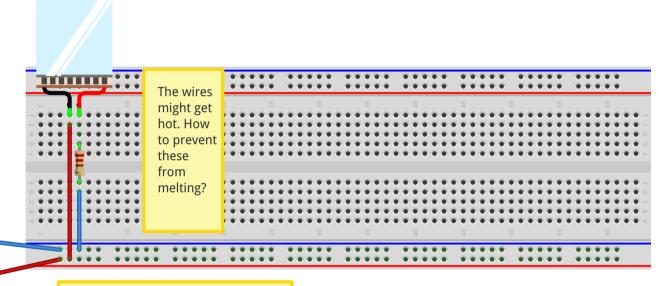
Which side of the Peltier element will heat up or cool in this setup?



External power supply Pin bottom left = +12 VDC Pin top left = GND Check this!

The orange connection will make the fan turn (upper pin = PS_ON, lower pin = GND)

Which resistor to use here?

We do have larger resistors to cope with higher currents.

Which resistor will hold?